 


Lab 5 Report

ALU

CENG 342 Digital Systems



Samuel Donovan

Samantha Pfeiffer

2021-02-16

OVERVIEW

The purpose of this lab was to build an ALU (Arithmetic Logic Unit) that combined our Adder/Subtractor and Barrel Shifter, designed in previous labs, with a Logic Unit into one module.

--- ALU ---

An ALU (Arithmetic Logic Unit) is responsible for the mathematical and logical operations within a CPU.

While some ALUs may contain complex circuits for things such as multiplication and trigonometric functions, the most basic ALU consists of an Adder/Subtractor (responsible for additions and subtractions), a Logic Unit (responsible for simple logical operations such as AND/OR/NOT), and a shifter (responsible for logical and arithmetic shift operations).

Every function has one or two inputs, **A** and **B**, and an output, **R**. Which operation is performed is dependent on the input **F**.

In addition to performing these operations on one or two inputs and providing the result, the ALU also commonly sets or clears flags in CPSR (current program status register), also known as a CCR (condition code register).

While the CPSR contains numerous status flags, the ALU is only concerned with 4: **N**egative, **Z**ero, **C**arry, and **O**Verflow. As not all flags are valid for every operation (e.g. AND will not have a carry), the status bits are cleared (set to 0) before each operation.

When an unsupported **F** code is given, **R** is set to all 0s, as are **N**, **Z**, **C**, and **V**.

Table 1 shows the valid **F** codes, as well as their defined operations and which status bits can be set as a result of the operation.

Table 1 ALU Operations

| <i>F</i> | Op | Description | <i>R</i> | Status Bits |
|----------|-----|------------------------|--------------------------|----------------|
| 0000 | ADD | Add | $A + B$ | N, Z, C_o, V |
| 0010 | ADC | Add w/ Carry | $A + B + C_i$ | N, Z, C_o, V |
| 0100 | SUB | Subtract | $A + \overline{B} + 1$ | N, Z, C_o, V |
| 0110 | SBC | Subtract w/ Carry | $A + \overline{B} + C_i$ | N, Z, C_o, V |
| 1001 | NOT | Bitwise NOT | \overline{B} | N, Z |
| 1011 | AND | Bitwise AND | $A \wedge B$ | N, Z |
| 1101 | OR | Bitwise OR | $A \vee B$ | N, Z |
| 1111 | XOR | Bitwise XOR | $A \oplus B$ | N, Z |
| 1000 | A | Pass A | A | N, Z |
| 1010 | LSL | Logical Shift Left | $A \ll B$ | N, Z, C_o, V |
| 1100 | LSR | Logical Shift Right | $A \gg B$ | N, Z, C_o |
| 1110 | ASR | Arithmetic Shift Right | $A \gg B(\text{signed})$ | N, Z, C_o |

DESIGN

All designs were made for a Nexys A7-100T (xc7a100tcsg324-1) FPGA board in VHDL using Vivado 2020.2.

--- LOGIC UNIT ---

The final functional block needed for the ALU consisted of four bitwise logic operations, referred to as the Logic Unit. The VHDL code for this block can be found in **Appendix B**. A `with select` statement is used to conditionally set a signal ***R*** based on the value of the input ***FUNC***. For each value of ***FUNC***, different bitwise logic is performed on inputs ***A*** and ***B***. The operations are listed in **Table 1**, and the corresponding ***FUNC*** values can be derived by looking at the center 2 bits ***F***. After ***R*** is set, it is assigned to the output ***Y***. ***R*** is used as an intermediary signal so that the ***N*** and ***Z*** flags can be set accordingly.

--- ALU ---

The ALU was designed using the adder/subtractor and barrel shifter from **Lab 4**, as well as the logic unit described above. As each of these units was tested and verified function prior to use in the ALU, combining them into a single unit was of relative ease. The VHDL code for the ALU is in **Appendix A**.

It was noticed that the input ***F***, which defines the function as seen in **Table 1**, followed the pattern that the first and last bits determined which sub-unit was used, and the two inner bits determined which operation was being performed within the units. Therefore, in the VHDL code ***F*** is divided into `FUNC_SEL` and `BLOCK_SEL` with the respective bits.

As seen in the VHDL code, after instantiating the three sub-units, their inputs are tied directly to the ALU's inputs (save for the `FUNCS`, which are tied to `FUNC_SEL`), and outputs are selectively tied to the ALU's outputs, dependent on `BLOCK_SEL`. As stated earlier, when an unsupported block is selected, the zero register

(defined in the code as `ZeroVec`) is returned.

--- TESTBENCH ---

Initially, the testbench was written to permute all possible combinations of ***A***, ***B***, ***C_i*** and ***FUNC***. This implementation wasted a large amount of time cycling through unused values of ***FUNC***, and was hard to navigate the valid values due to the sheer quantity ***A*** and ***B*** values. The produced waveform was long and difficult to read, and thus was not that useful for verifying the functionality of the ALU design.

Therefore, instead of checking every single possible value, a testbench was created to cycle through all values of ***FUNC*** and ***C_i*** with random constant values of ***A*** and ***B***. This way it can easily be seen that each function of the ALU works as expected.

The VHDL code for the testbench can be found in **Appendix D**.

--- CONSTRAINTS ---

The constraints file can be found in **Appendix E**. Switches 0 to 3 were used for the four input bits of ***A*** and switches 4 to 7 for the input bits of ***B***. The four bits of ***F*** were mapped to switches 12 to 15 for readability. The final input, ***C_{in}*** was set to the center push button, or BTNC. For outputs, LEDs 0 to 3 were used to display the four bits of ***R***. Then ***N***, ***Z***, ***C_{out}***, and ***V*** were set to LEDs 11, 10, 9, and 8 respectively.

Figure 1 Simulation Results for FUNC = “0000” to FUNC = “1000”


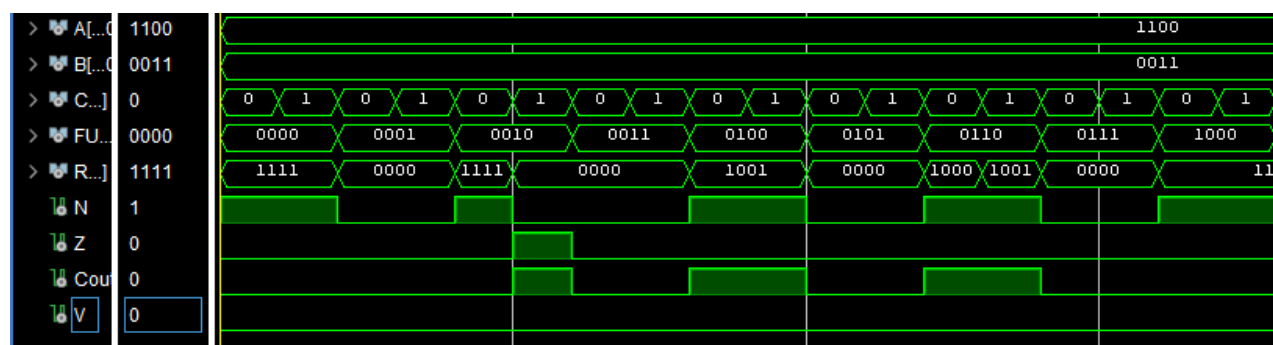


Figure 2 Simulation Results for FUNC = “1000” to FUNC = “1111”

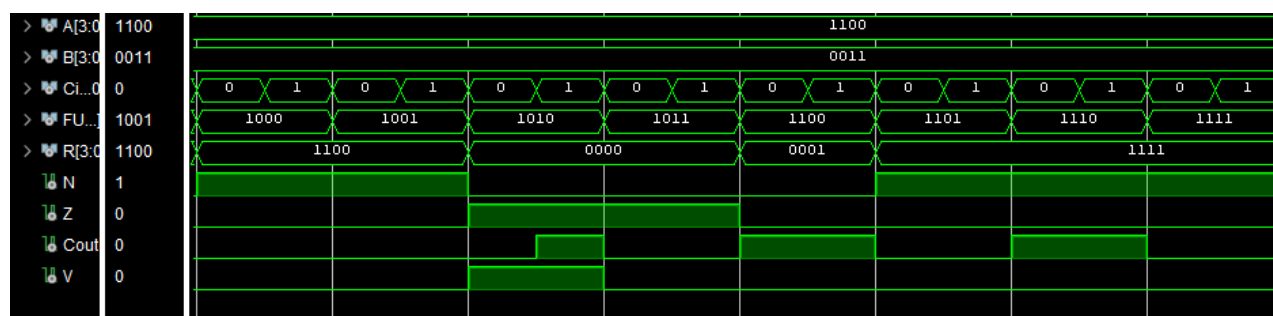

SYNTHESIS RESULTS

Figure 3 Synthesis of Bitwise XOR



Figure 4 Synthesis of Add with Carry


 


Figure 5 Synthesis of LSL

 

ISSUES ENCOUNTERED

The only issue of note that we encountered was that the barrel shifter from **Lab 4** took a single input `N_Layers`, which determined the shifter's `BUS_SIZE` internally. While this made sense previously, when using the shifter for the ALU, this design choice made it rather confusing what was happening internally. To fix this, the barrel shifter was slightly modified to take both `N_LAYERS` and `BUS_SIZE`. However, as `N_LAYERS` needed to conform to $\log_2(BUS_SIZE)$, we needed to use `IEEE.MATH._REAL` and `IEEE.NUMERIC_STD` libraries to generically compute the number of layers (held in the constant `SHIFTER_LAYERS` in the ALU VHDL code in **Appendix A**), as the \log_2 operation was not supported by default.

We also encountered an issue where our **R** value for the ALU was incorrectly being set to **X** (undefined). The cause of this was quickly identified to be **R** being incorrectly tied directly to a sub-unit's output, rather than that unit's respective output signal occupying the output port.

CONCLUSIONS

Thanks to our previous testing and functionality verification of the adder/subtractor and barrel shifter, designing a functionally ALU was as simple as including a library. Had those units been dysfunctional or not been written in a generalizable and maintainable way, we would have spent many more hours than needed completing this lab.

While we did not test every possible input combination to the ALU, we believe our test data is random and representative enough to prove it's functionality.

APPENDIX A: ALU VHDL Code (alu.vhdl)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.MATH_REAL.ALL;
use IEEE.NUMERIC_STD.ALL;

entity alu is
    generic(BUS_SIZE: natural :=1);
    Port (
        A, B: in std_logic_vector(BUS_SIZE-1 downto 0);
        F: in std_logic_vector(3 downto 0);
        Cin: in std_logic;
        R: out std_logic_vector(BUS_SIZE-1 downto 0);
        N,Z,Cout,V: out std_logic
    );
end alu;

architecture behavioral of alu is
    signal BLOCK_SEL: std_logic_vector(1 downto 0);
    signal FUNC_SEL: std_logic_vector(1 downto 0);
    signal N_mux,Z_mux,Cout_mux,V_mux : std_logic_vector(2
downto 0);
    signal SUM, SHIFTED, BITWISE : std_logic_vector(BUS_SIZE-1
downto 0);
    signal ZeroVec : STD_LOGIC_VECTOR(BUS_SIZE-1 downto 0);
    constant SHIFTER_LAYERS: natural :=
natural(ceil(log2(real(BUS_SIZE)))));
    signal SHFT_AMT : STD_LOGIC_VECTOR(SHIFTER_LAYERS-1 downto
0);
begin
    ZeroVec <= (others => '0');
    FUNC_SEL <= F(2 downto 1);
    BLOCK_SEL <= F(3) & F(0);

    addsub: entity work.addsub (behavioral)
        generic map(BUS_SIZE=>BUS_SIZE)
        port
map(A=>A,B=>B,Cin=>Cin,S=>SUM,N=>N_mux(0),Z=>Z_mux(0),V=>V_mux(
0),Cout=>Cout_mux(0),FUNC=>FUNC_SEL);
```

```

    logic_unit: entity work.logic_unit (behavioral)
        generic map(BUS_SIZE=>BUS_SIZE)
        port map(A=>A,B=>B,Y=>BITWISE, N=>N_mux(1),
Z=>Z_mux(1), FUNC=>FUNC_SEL);
        V_mux(1) <= '0';
        Cout_mux(1) <= '0';
        shifter: entity work.shifter (behavioral)
            generic map(BUS_SIZE=>BUS_SIZE,
N_LAYERS=>SHIFTER_LAYERS)
            port map(rIN=>A, rOUT=>SHIFTED,
shftAmt=>B(SHIFTER_LAYERS-1 downto
0),N=>N_mux(2),Z=>Z_mux(2),V=>V_mux(2),Cout=>Cout_mux(2),FUNC=>
FUNC_SEL);
            SHFT_AMT <= B(SHIFTER_LAYERS-1 downto 0);

with BLOCK_SEL select
    R <= SUM      when "00", --ADD/SUB
        BITWISE when "11", --Logic
        SHIFTED  when "10", --Shifter
        ZeroVec  when others; --Reserved (Return 0)

with BLOCK_SEL select
    N <= N_mux(0)   when "00", --ADD/SUB
        N_mux(1)   when "11", --Logic
        N_mux(2)   when "10", --Shifter
        '0'        when others; --Reserved (Return 0)

with BLOCK_SEL select
    Z <= Z_mux(0)   when "00", --ADD/SUB
        Z_mux(1)   when "11", --Logic
        Z_mux(2)   when "10", --Shifter
        '0'        when others; --Reserved (Return 0)

with BLOCK_SEL select
    V <= V_mux(0)   when "00", --ADD/SUB
        V_mux(1)   when "11", --Logic
        V_mux(2)   when "10", --Shifter
        '0'        when others; --Reserved (Return 0)

with BLOCK_SEL select
    Cout <= Cout_mux(0) when "00", --ADD/SUB

```

```
        '0'          when "11", --Logic  
        Cout_mux(0)  when "10", --Shifter  
        '0'          when others; --Reserved (Return 0)  
  
end behavioral;
```

APPENDIX B: Logic Unit VHDL Code (logic_unit.vhdl)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.all;

entity logic_unit is
    generic(BUS_SIZE: natural :=1);
    Port (
        A, B: in std_logic_vector(BUS_SIZE-1 downto 0);
        Y: out std_logic_vector(BUS_SIZE-1 downto 0);
        N,Z: out std_logic;
        FUNC: in std_logic_vector(1 downto 0)
    );
end logic_unit;

architecture behavioral of logic_unit is
    signal R: std_logic_vector(BUS_SIZE-1 downto 0);
begin

    with FUNC select
        R <= not(B)      when "00",
            (A and B)    when "01",
            (A or B)     when "10",
            (A xor B)    when others;

    Y <= R;
    N <= R(BUS_SIZE-1);
    Z <= '1' when (R = 0) else '0';
end behavioral;
```

APPENDIX C: Modified Barrel Shifter VHDL Code (shifter.vhdl)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.all;
use IEEE.NUMERIC_STD.ALL;

entity shifter is
    generic(BUS_SIZE: natural := 8;
           N_LAYERS: natural := 3); --N-LAYERS =
log2(BUS_SIZE)
    port(rIN : in STD_LOGIC_VECTOR(BUS_SIZE-1 downto 0);
         rOUT : out STD_LOGIC_VECTOR(BUS_SIZE-1 downto 0);
         shftAmnt : in STD_LOGIC_VECTOR(N_LAYERS-1 downto 0);
         N,Z,V,Cout : out STD_LOGIC;
         FUNC : in STD_LOGIC_VECTOR (1 downto 0)
         );
end shifter;

architecture behavioral of shifter is
    type STD_LOGIC_VECTOR_2 is array (integer range<>) of
STD_LOGIC_VECTOR(BUS_SIZE-1 downto 0);
    signal A : STD_LOGIC_VECTOR_2(N_LAYERS-1 downto 0);
    signal B : STD_LOGIC_VECTOR_2(N_LAYERS-1 downto 0);
    signal Y : STD_LOGIC_VECTOR_2(N_LAYERS-1 downto -1);
    signal ZeroVec : STD_LOGIC_VECTOR(BUS_SIZE-1 downto 0);
    signal OneVec : STD_LOGIC_VECTOR(BUS_SIZE-1 downto 0);
    constant NOP: STD_LOGIC_VECTOR(1 downto 0) := "00";
    constant LSL: STD_LOGIC_VECTOR(1 downto 0) := "01";
    constant LSR: STD_LOGIC_VECTOR(1 downto 0) := "10";
    constant ASR: STD_LOGIC_VECTOR(1 downto 0) := "11";
begin
    ZeroVec <= (others => '0');
    OneVec <= (others => '1');
    Y(-1) <= rIN;

    muxes: for layer in N_LAYERS-1 downto 0 generate
        muxN: entity work.mux (behavioral)
            generic map(BUS_SIZE=>BUS_SIZE)
            port map(A=>A(layer),
                    B=> B(layer),
```

```
SEL=>shftAmnt(layer),
Y=>Y(layer));
A(layer) <= Y(layer-1);
B(layer) <= Y(layer-1)(BUS_SIZE-1-2**layer downto 0) &
ZeroVec(2**layer-1 downto 0) when FUNC=LSL else
ZeroVec(2**layer-1 downto 0) &
Y(layer-1)(BUS_SIZE-1 downto 2**layer) when FUNC=LSR else
ZeroVec(2**layer-1 downto 0) &
Y(layer-1)(BUS_SIZE-1 downto 2**layer) when (FUNC=ASR and
rIN(BUS_SIZE-1)='0') else
OneVec(2**layer-1 downto 0) &
Y(layer-1)(BUS_SIZE-1 downto 2**layer) when (FUNC=ASR and
rIN(BUS_SIZE-1)='1') else
A(layer); --No shift
end generate muxes;

rOUT <= Y(N_LAYERS-1);
N <= Y(N_LAYERS-1)(BUS_SIZE-1);
Z <= '1' when Y(N_LAYERS-1) = 0 else '0';
V <= '1' when Y(N_LAYERS-1)(BUS_SIZE-1) /= rIN(BUS_SIZE-1)
AND FUNC=LSL else '0';
Cout <= rIN(BUS_SIZE - 1 - to_integer(unsigned(shftAmnt)))
when shftAmnt /= 0 AND FUNC /= NOP else '0';
end behavioral;
```

APPENDIX D: ALU Testbench VHDL Code (alu_testbench.vhdl)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity alu_testbench is
end alu_testbench;

architecture Behavioral of alu_testbench is
    constant BUS_SIZE: natural := 4;
    signal A, B, R: std_logic_vector(BUS_SIZE-1 downto 0);
    signal FUNC : std_logic_vector(3 downto 0);
    signal Cin : std_logic_vector(0 to 0);
    signal N,Z,Cout,V: std_logic;
begin

    ALU: entity work.alu (behavioral)
        generic map (BUS_SIZE=>BUS_SIZE)
        port map (A=>A,B=>B,F=>FUNC,Cin=>Cin(0),
            R=>R,N=>N,Z=>Z,V=>V,Cout=>Cout);

    test: process
        variable i, j, k: integer;
    begin

        A <= "1100";
        B <= "0011";
        FUNC <= (others => '0');
        Cin <= (others => '0');

        for i in 0 to 15 loop
            Cin <= "0";
            FUNC <= std_logic_vector(TO_UNSIGNED(i,4));
            wait for 1ns;
            Cin <= "1";
            wait for 1ns;
        end loop;
    end process;
end Behavioral;
```


APPENDIX E: Contains File (alu_constraints.xdc)

```
##Switches
set_property -dict { PACKAGE_PIN J15      IOSTANDARD LVCMOS33 }
[get_ports { A[0] }];
set_property -dict { PACKAGE_PIN L16      IOSTANDARD LVCMOS33 }
[get_ports { A[1] }];
set_property -dict { PACKAGE_PIN M13      IOSTANDARD LVCMOS33 }
[get_ports { A[2] }];
set_property -dict { PACKAGE_PIN R15      IOSTANDARD LVCMOS33 }
[get_ports { A[3] }];
set_property -dict { PACKAGE_PIN R17      IOSTANDARD LVCMOS33 }
[get_ports { B[0] }];
set_property -dict { PACKAGE_PIN T18      IOSTANDARD LVCMOS33 }
[get_ports { B[1] }];
set_property -dict { PACKAGE_PIN U18      IOSTANDARD LVCMOS33 }
[get_ports { B[2] }];
set_property -dict { PACKAGE_PIN R13      IOSTANDARD LVCMOS33 }
[get_ports { B[3] }];
set_property -dict { PACKAGE_PIN H6       IOSTANDARD LVCMOS33 }
[get_ports { F[0] }];
set_property -dict { PACKAGE_PIN U12      IOSTANDARD LVCMOS33 }
[get_ports { F[1] }];
set_property -dict { PACKAGE_PIN U11      IOSTANDARD LVCMOS33 }
[get_ports { F[2] }];
set_property -dict { PACKAGE_PIN V10      IOSTANDARD LVCMOS33 }
[get_ports { F[3] }];

## LEDs
set_property -dict { PACKAGE_PIN H17      IOSTANDARD LVCMOS33 }
[get_ports { R[0] }];
set_property -dict { PACKAGE_PIN K15      IOSTANDARD LVCMOS33 }
[get_ports { R[1] }];
set_property -dict { PACKAGE_PIN J13      IOSTANDARD LVCMOS33 }
[get_ports { R[2] }];
set_property -dict { PACKAGE_PIN N14      IOSTANDARD LVCMOS33 }
[get_ports { R[3] }];
set_property -dict { PACKAGE_PIN V16      IOSTANDARD LVCMOS33 }
[get_ports { V }];
```

```
set_property -dict { PACKAGE_PIN T15      IOSTANDARD LVCMOS33 }  
[get_ports { Cout }];  
set_property -dict { PACKAGE_PIN U14      IOSTANDARD LVCMOS33 }  
[get_ports { Z }];  
set_property -dict { PACKAGE_PIN T16      IOSTANDARD LVCMOS33 }  
[get_ports { N }];  
  
## Buttons  
set_property -dict { PACKAGE_PIN N17      IOSTANDARD LVCMOS33 }  
[get_ports { Cin }];
```