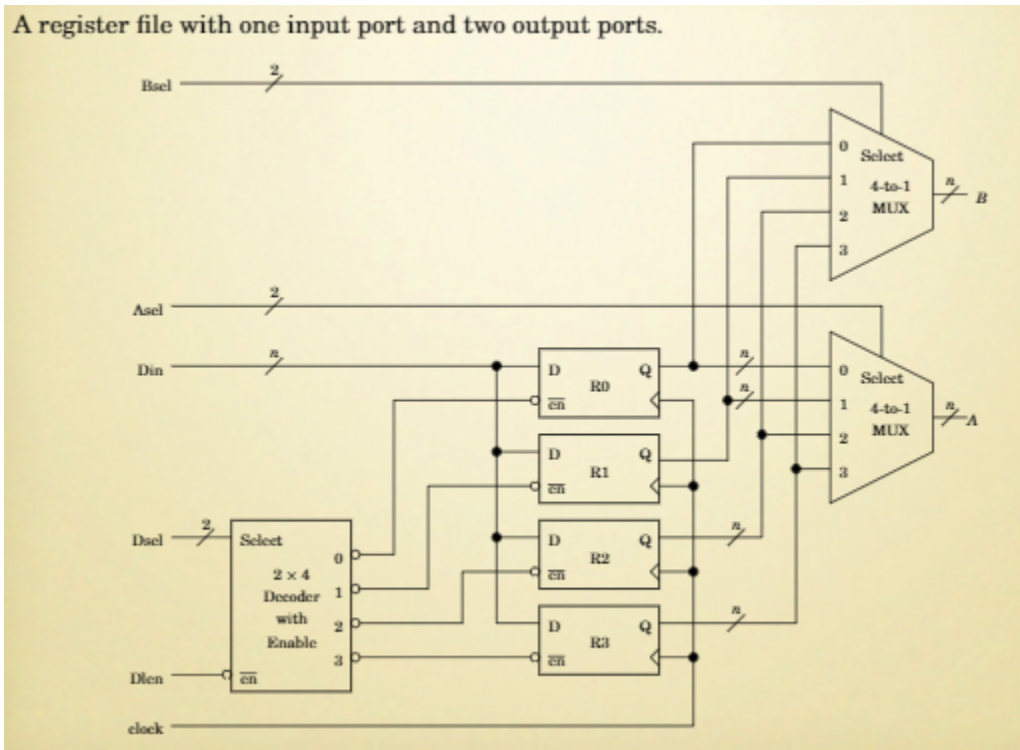


Lab 7 Report

Register File

CENG 342 Digital Systems



Samuel Donovan

Samantha Pfeiffer

2021-03-15


OVERVIEW

The purpose of this lab was to build a register file that will serve as the primary SRAM for the CPU.

--- REGISTER ---

A register is a number of flip flops that are accessed in unison. A register can be written to, or read from. Registers commonly also have reset capability. See figure below.

Figure 1 Register Diagram

 

--- REGISTER FILE ---

The register file consists of a number of registers that can be selectively written to and read from. The file consists of 6 inputs and 2 outputs.

Table 1 Register File I/O

Name	In/Out	Size	Description
Reset	In	1	Clears all registers in the file
CLK	In	1	Write is triggered on rising edge
WriteEnable	In	1	Enables writing to the registers
InputSel	In	$\log_2(\# \text{ of Reg})$	Write register select
Input	In	Register Size	Write input
OutputASel	In	$\log_2(\# \text{ of Reg})$	Read Output A register select
OutputBSel	In	$\log_2(\# \text{ of Reg})$	Read Output B register select
OutputA	Out	Register Size	Read Output A
OutputB	Out	Register Size	Read Output B

As can be seen in **Table 1**, two registers can be read at once from the write file.

DESIGN

All designs were made for a Nexys A7-100T (xc7a100tcsg324-1) FPGA board in VHDL using Vivado 2020.2.

--- REGISTER ---

A generic n -bit register was designed using a simple `process`, where the state of the output (`q`) is conditionally set to the input (`d`) on `clk`'s rising edge, or to 0 when `reset`.

See **Appendix A**.

--- REGISTER FILE ---

For the register file, two generics are taken as input parameters: `REG_SIZE`, and `N_REG`. Save for that, the port scheme is identical to that seen in **Table 1**.

Some math is done to compute $\log_2(\text{REG_SIZE})$ which is then used as the `sel` `STD_LOGIC_VECTOR`'s sizes.

During operation, the `sel` `STD_LOGIC_VECTORS` are converted into unsigned integers to be used as indexes in the register array, which are selectively tied to the input and outputs.

See **Appendix D**.

--- CONSTRAINTS ---

For synthesizing a 4-bit register, four switches were set to be its input, and a push button was tied to its reset. As is required by Vivado/VHDL, the internal clock was tied to `CLK`. Four LEDs were tied to `q`. See **Appendix C** for the .xdc file.

For synthesizing a 4-bit register file with 8 registers, four switches were again set to be its input, and a push button was tied to its reset, and the internal clock was again used as `CLK`. Additionally, for each of the three selects (`InputSel`, `OutputB`, `OutputASel`), three switches were used. Eight LEDs were divided between `OutputA` and `OutputB`. See **Appendix F** for the .xdc file.

SIMULATION RESULTS

Figure 2 Register Sim Results (REG_SIZE = 4) [Appendix B]


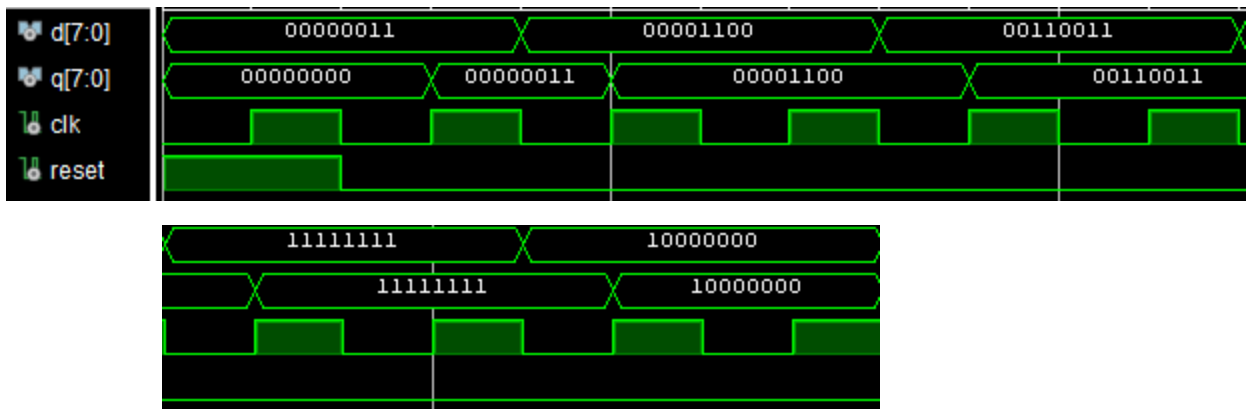


Figure 3 Register File Sim Results (REG_SIZE = 8, N_REGS = 10) [Appendix F]

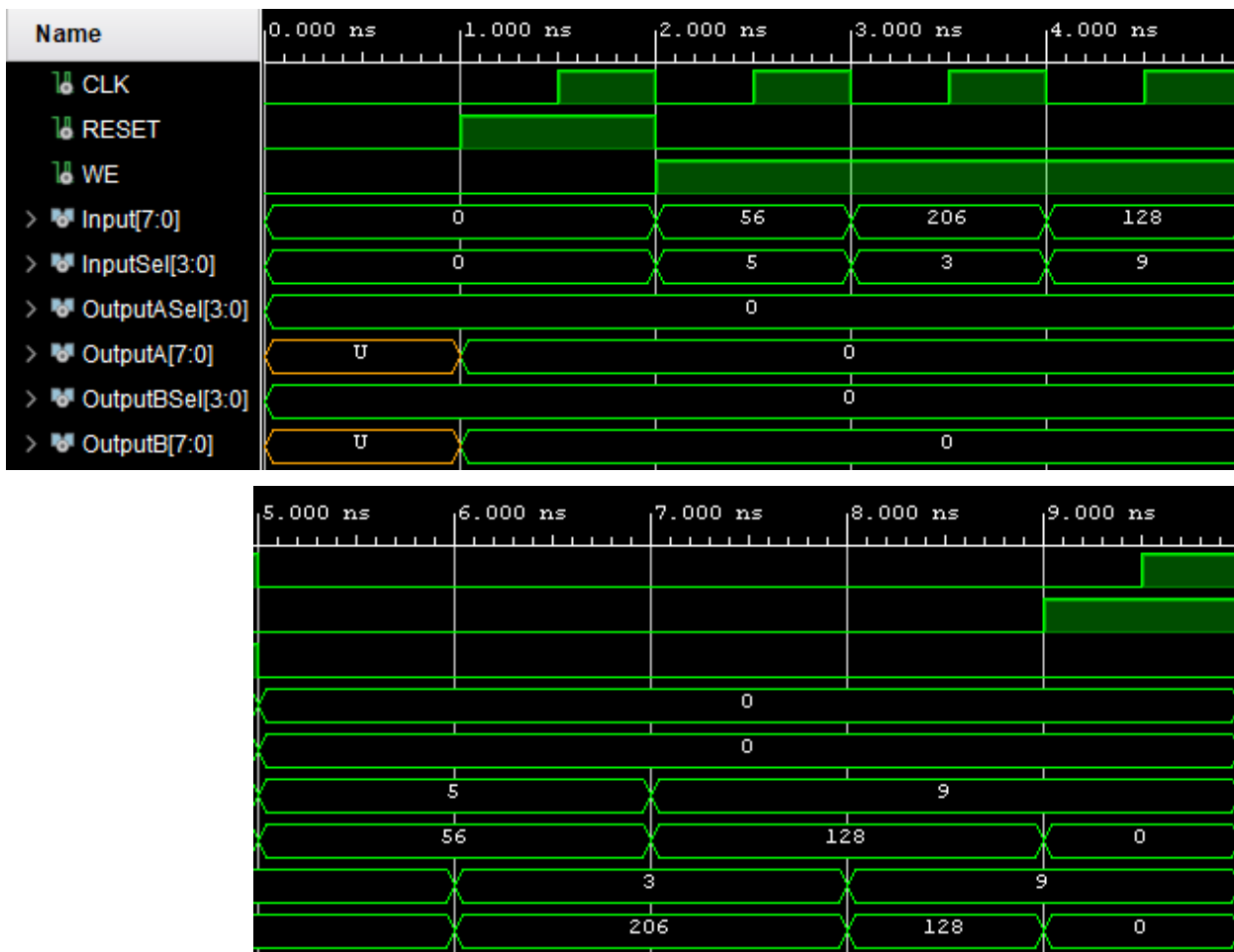

SYNTHESIS RESULTS

Figure 4 Register Synth - Output Displaying '1001'

 


Figure 5 Register Synth - Output Displaying '1111'

 


Figure 6 Register File Synth - A and B Displaying Different Registers

 


Figure 7 Register File Synth - A and B Displaying the Same Register

 
 


Figure 8 Register File Synth - Reset Button Clears Output

ISSUES ENCOUNTERED

During synthesis, it was discovered that the `CLK` variable could not be tied to switch, and must be tied to the inner clock of the board due to the way that VHDL's `CLK` variable works.

CONCLUSIONS

Given our familiarity with registers and flip-flops , the simplicity of this lab meant writing and simulating our components took very little time.

While the single register was easy to physically test, due to the number bits inputted and outputted from the register file it proved a bit confusing to test physically. However, once testing was complete, both components were found to work as expected.

APPENDIX A: Generic Register VHDL Code (gen_register.vhdl)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity gen_register is
  generic(N: integer := 8);
  Port (
    clk, reset: in std_logic;
    d: in std_logic_vector((N-1) downto 0);
    q: out std_logic_vector((N-1) downto 0)
  );
end gen_register;

architecture Behavioral of gen_register is
begin
  process(clk, reset)
  begin
    if (reset='1') then
      q <= (others=>'0');
    elsif(clk'event and clk='1') then
      q <= d;
    end if;
  end process;
end Behavioral;
```

APPENDIX B: Generic Register Testbench VHDL Code (gen_register_testbench.vhdl)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity gen_reg_testbench is
end gen_reg_testbench;

architecture Behavioral of gen_reg_testbench is
    component gen_register
        PORT(
            clk, reset: in std_logic;
            d: in std_logic_vector(7 downto 0);
            q: out std_logic_vector(7 downto 0)
        );
    end component;

    signal d,q: std_logic_vector(7 downto 0) := (others => '0');
    signal clk: std_logic := '0';
    signal reset: std_logic := '1';
    constant clk_period : time := 20ns;

begin

    EightBitReg: entity work.gen_register (Behavioral)
        generic map(N=>8)
        port map(clk=>clk, d=>d, q=>q, reset=>reset);

    clk_process: process
    begin
        clk <= '0';
        wait for clk_period/2;
        clk <= '1';
        wait for clk_period/2;
    end process;

    sim_proc: process
    begin
```



```
    reset <= '0' after 20ns;
    d <= "00000011";
    wait until falling_edge(clk);
    wait until falling_edge(clk);
    d <= "00001100";
    wait until falling_edge(clk);
    wait until falling_edge(clk);
    d <= "00110011";
    wait until falling_edge(clk);
    wait until falling_edge(clk);
    d <= "11111111";
    wait until falling_edge(clk);
    wait until falling_edge(clk);
    d <= "10000000";
    wait until falling_edge(clk);
    wait until falling_edge(clk);
    wait;
end process;

end Behavioral;
```

APPENDIX C: Generic Register Constraints (gen_reg_constraints.xdc)

```
## Clock signal
set_property -dict { PACKAGE_PIN E3      IOSTANDARD LVCMOS33 }
[get_ports { clk }]; #IO_L12P_T1_MRCC_35 Sch=clk100mhz

##Switches
set_property -dict { PACKAGE_PIN J15      IOSTANDARD LVCMOS33 }
[get_ports { d[0] }];
set_property -dict { PACKAGE_PIN L16      IOSTANDARD LVCMOS33 }
[get_ports { d[1] }];
set_property -dict { PACKAGE_PIN M13      IOSTANDARD LVCMOS33 }
[get_ports { d[2] }];
set_property -dict { PACKAGE_PIN R15      IOSTANDARD LVCMOS33 }
[get_ports { d[3] }];

## LEDs
set_property -dict { PACKAGE_PIN H17      IOSTANDARD LVCMOS33 }
[get_ports { q[0] }];
set_property -dict { PACKAGE_PIN K15      IOSTANDARD LVCMOS33 }
[get_ports { q[1] }];
set_property -dict { PACKAGE_PIN J13      IOSTANDARD LVCMOS33 }
[get_ports { q[2] }];
set_property -dict { PACKAGE_PIN N14      IOSTANDARD LVCMOS33 }
[get_ports { q[3] }];

##Buttons
set_property -dict { PACKAGE_PIN N17      IOSTANDARD LVCMOS33 }
[get_ports { reset }];
```

APPENDIX D: Generic Register File VHDL Code (gen_register_file.vhdl)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.MATH_REAL.ALL;
use IEEE.NUMERIC_STD.ALL;

entity gen_reg_file is
    generic(
        REG_SIZE: integer := 8;
        N_REGS: integer := 2
    );
    Port (
        clk, reset, writeEnable: in std_logic;
        InputSel: in
            std_logic_vector(natural(ceil(log2(real(N_REGS))))-1 downto 0);
        Input: in std_logic_vector(REG_SIZE-1 downto 0);
        OutputASel, OutputBSel: in
            std_logic_vector(natural(ceil(log2(real(N_REGS))))-1 downto 0);
        OutputA, OutputB: out std_logic_vector (REG_SIZE-1
            downto 0)
    );
end gen_reg_file;

architecture Behavioral of gen_reg_file is
    type REG_ARR is array(N_REGS-1 downto 0) of
        std_logic_vector(REG_SIZE-1 downto 0);

    signal regs: REG_ARR;

begin
    process(clk, reset)
    begin
        if(reset = '1') then
            regs <= (others=>(others=>'0')); --Clear all
            registers
        elsif(clk'event and clk='1') then
            if writeEnable='1' then
                regs(to_integer(unsigned(InputSel)))<= Input;
            end if;
        end if;
    end process;
end Behavioral;
```

```
        end process;  
        OutputA <= regs(to_integer(unsigned(OutputASel)));  
        OutputB <= regs(to_integer(unsigned(OutputBSel)));  
    end Behavioral;
```

APPENDIX E: Generic Register File Testbench VHDL Code (gen_register_file_testbench.vhdl)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.MATH_REAL.ALL;
use IEEE.NUMERIC_STD.ALL;
use STD.ENV.STOP;

entity gen_reg_file_testbench is
end gen_reg_file_testbench;

architecture Behavioral of gen_reg_file_testbench is
    constant REGSIZE: integer := 8;
    constant NREGS: integer := 16;
    constant SELSIZE: natural :=
natural(ceil(log2(real(NREGS))));
    signal CLK, RESET, WE: STD_LOGIC := '0';
    signal InputSel, OutputASel, OutputBSel:
STD_LOGIC_VECTOR(SELSize-1 downto 0);
    signal Input, OutputA, OutputB : STD_LOGIC_VECTOR(REGSIZE-1
downto 0);

begin

reg_file: entity work.gen_reg_file (behavioral)
    generic map(REG_SIZE=>REGSIZE, N_REGS=>NREGS)
    port map(
        clk=>CLK,
        reset=>RESET,
        writeEnable=>WE,
        InputSel=>InputSel,
        Input=>Input,
        OutputASel=>OutputASel,
        OutputBSel=>OutputBSel,
        OutputA=>OutputA,
        OutputB=>OutputB
    );

testProc: process
```



```
begin
    --Set signals 0
    CLK <= '0';
    RESET <= '0';
    WE <= '0';
    InputSel <= (others => '0');
    Input <= (others => '0');
    OutputASel <= (others => '0');
    OutputBSel <= (others => '0');
    wait for 1ns;

    --Reset
    RESET <= '1';
    wait for 0.5ns;
    CLK <= '1';
    wait for 0.5ns;
    CLK <= '0';
    RESET <= '0';

    --Write 56 to reg 5
    WE <= '1';
    Input <= std_logic_vector(to_unsigned(56, REGSIZE));
    InputSel <= std_logic_vector(to_unsigned(5, SELSIZE));
    wait for 0.5ns;
    CLK <= '1';
    wait for 0.5ns;
    CLK <= '0';
    Input <= std_logic_vector(to_unsigned(0, REGSIZE));
    InputSel <= std_logic_vector(to_unsigned(0, SELSIZE));

    --Write 206 to reg 3
    WE <= '1';
    Input <= std_logic_vector(to_unsigned(206, REGSIZE));
    InputSel <= std_logic_vector(to_unsigned(3, SELSIZE));
    wait for 0.5ns;
    CLK <= '1';
    wait for 0.5ns;
    CLK <= '0';
    WE <= '0';
    Input <= std_logic_vector(to_unsigned(0, REGSIZE));
    InputSel <= std_logic_vector(to_unsigned(0, SELSIZE));
```

```
--Write 128 to reg 9
WE <= '1';
Input <= std_logic_vector(to_unsigned(128, REGSIZE));
InputSel <= std_logic_vector(to_unsigned(9, SELSIZE));
wait for 0.5ns;
CLK <= '1';
wait for 0.5ns;
CLK <= '0';
WE <= '0';
Input <= std_logic_vector(to_unsigned(0, REGSIZE));
InputSel <= std_logic_vector(to_unsigned(0, SELSIZE));

--Read reg 5 to output A
OutputASel <= std_logic_vector(to_unsigned(5, SELSIZE));
wait for 1ns;

--Read reg 3 to output
OutputBSel <= std_logic_vector(to_unsigned(3, SELSIZE));
wait for 1ns;

--Read reg 9 to output A
OutputASel <= std_logic_vector(to_unsigned(9, SELSIZE));
wait for 1ns;

--Read reg 9 to output B
OutputBSel <= std_logic_vector(to_unsigned(9, SELSIZE));
wait for 1ns;

--Reset
RESET <= '1';
wait for 0.5ns;
CLK <= '1';
wait for 0.5ns;
CLK <= '0';
RESET <= '0';

stop;
end process;
end Behavioral;
```


APPENDIX F: Generic Register File Constraints File

(gen_reg_file_constraints.xdc)

```
## Clock signal
set_property -dict { PACKAGE_PIN E3      IOSTANDARD LVCMOS33 }
[get_ports { clk }]; #IO_L12P_T1_MRCC_35 Sch=clk100mhz

##Switches
set_property -dict { PACKAGE_PIN J15      IOSTANDARD LVCMOS33 }
[get_ports { Input[0] }];
set_property -dict { PACKAGE_PIN L16      IOSTANDARD LVCMOS33 }
[get_ports { Input[1] }];
set_property -dict { PACKAGE_PIN M13      IOSTANDARD LVCMOS33 }
[get_ports { Input[2] }];
set_property -dict { PACKAGE_PIN R15      IOSTANDARD LVCMOS33 }
[get_ports { Input[3] }];
set_property -dict { PACKAGE_PIN R17      IOSTANDARD LVCMOS33 }
[get_ports { InputSel[0] }];
set_property -dict { PACKAGE_PIN T18      IOSTANDARD LVCMOS33 }
[get_ports { InputSel[1] }];
set_property -dict { PACKAGE_PIN U18      IOSTANDARD LVCMOS33 }
[get_ports { InputSel[2] }];
set_property -dict { PACKAGE_PIN R13      IOSTANDARD LVCMOS33 }
[get_ports { OutputASel[0] }];
set_property -dict { PACKAGE_PIN T8       IOSTANDARD LVCMOS18 }
[get_ports { OutputASel[1] }];
set_property -dict { PACKAGE_PIN U8       IOSTANDARD LVCMOS18 }
[get_ports { OutputASel[2] }];
set_property -dict { PACKAGE_PIN R16      IOSTANDARD LVCMOS33 }
[get_ports { OutputBSel[0] }];
set_property -dict { PACKAGE_PIN T13      IOSTANDARD LVCMOS33 }
[get_ports { OutputBSel[1] }];
set_property -dict { PACKAGE_PIN H6       IOSTANDARD LVCMOS33 }
[get_ports { OutputBSel[2] }];
#set_property -dict { PACKAGE_PIN U12      IOSTANDARD LVCMOS33 }
[get_ports { SW[13] }]; #IO_L
set_property -dict { PACKAGE_PIN U11      IOSTANDARD LVCMOS33 }
[get_ports { clk }];
set_property -dict { PACKAGE_PIN V10      IOSTANDARD LVCMOS33 }
[get_ports { writeEnable }];
```

```
## LEDs
set_property -dict { PACKAGE_PIN H17      IOSTANDARD LVCMOS33 }
[get_ports { OutputA[0] }];
set_property -dict { PACKAGE_PIN K15      IOSTANDARD LVCMOS33 }
[get_ports { OutputA[1] }];
set_property -dict { PACKAGE_PIN J13      IOSTANDARD LVCMOS33 }
[get_ports { OutputA[2] }];
set_property -dict { PACKAGE_PIN N14      IOSTANDARD LVCMOS33 }
[get_ports { OutputA[3] }];
set_property -dict { PACKAGE_PIN R18      IOSTANDARD LVCMOS33 }
[get_ports { OutputB[0] }];
set_property -dict { PACKAGE_PIN V17      IOSTANDARD LVCMOS33 }
[get_ports { OutputB[1] }];
set_property -dict { PACKAGE_PIN U17      IOSTANDARD LVCMOS33 }
[get_ports { OutputB[2] }];
set_property -dict { PACKAGE_PIN U16      IOSTANDARD LVCMOS33 }
[get_ports { OutputB[3] }];

##Buttons
set_property -dict { PACKAGE_PIN N17      IOSTANDARD LVCMOS33 }
[get_ports { reset }];
```